

# Robotics From Scratch

## Lesson 4: Electricity Basics - Summary Handout

### Key Concepts

#### Fundamental Definitions

- **Voltage (V):** Electrical "pressure" in Volts
- **Current (I):** Flow of charge in Amperes
- **Resistance (R):** Opposition to flow in Ohms ( $\Omega$ )
- **Power (P):** Energy rate in Watts

#### Essential Formulas

$$V = I \cdot R \quad (\text{Ohm's Law})$$

$$P = I \cdot V \quad (\text{Watt's Law})$$

$$P = I^2 \cdot R = \frac{V^2}{R}$$

#### SI Prefixes

Name	Symbol	Value
milli	m	$10^{-3}$
micro	$\mu$	$10^{-6}$
kilo	k	$10^3$
mega	M	$10^6$

#### AC vs DC

**DC:** Current flows one direction (batteries, electronics)

**AC:** Current reverses direction (wall outlets, 60Hz)

#### Circuit Basics

- Circuit = closed loop
- Ground = 0V reference
- Polarity matters!

### Practice Problems

#### Problem 1: Basic Ohm's Law

9V battery,  $470\Omega$  resistor. Find:

- a) Current
- b) Power dissipated

#### Problem 2: Find Resistance

Motor draws 1.5A from 12V supply. Find motor resistance.

#### Problem 3: Series Circuit

Resistors:  $100\Omega$ ,  $220\Omega$ ,  $330\Omega$  in series, 12V battery. Find:

- a) Total resistance
- b) Current
- c) Voltage drop across each

$$\text{Hint: } R_{total} = R_1 + R_2 + R_3$$

#### Problem 4: Power & Battery Life

Motor: 2.5A from 6V battery (2000mAh capacity)

- a) Power consumed?
- b) Run time?

# Python Programming Exercises

## Exercise 5: Ohm's Law Calculator

Create a program that calculates V, I, or R given the other two values. Include unit conversions (mA ↔ A, kΩ ↔ Ω).

**Starter Code:**

```
1 def calculate_voltage(current, resistance):
2     return current * resistance
3
4 def calculate_current(voltage, resistance):
5     return voltage / resistance
6
7 def calculate_resistance(voltage, current):
8     return voltage / current
9
10 # TODO: Add user input, menu, unit conversions, error handling
11 print("=== Ohm's Law Calculator ===")
```

## Exercise 6: Series Resistor Calculator

Program that accepts resistor list, calculates total resistance, current, voltage drops, and displays formatted table.

**Example Output:**

Resistors: [100, 220, 330] ohms | Supply: 12V

Total R: 650Ω | Current: 18.5 mA

Resistor	Voltage	Power
100 Ω	1.85 V	0.034 W
220 Ω	4.07 V	0.075 W
330 Ω	6.11 V	0.113 W

## Further Study Topics

### Series vs Parallel Circuits

#### Series Circuits:

- Components share same current
- Voltages add:  $V_{total} = V_1 + V_2 + \dots$
- Resistances add:  $R_{total} = R_1 + R_2 + \dots$
- Used in: voltage dividers, Christmas lights
- Drawback: One break stops all
- **Batteries in series:** Voltages add (e.g., two 1.5V AA batteries = 3V)

#### Parallel Circuits:

- Components share same voltage
- Currents add:  $I_{total} = I_1 + I_2 + \dots$
- Reciprocal:  $\frac{1}{R_{total}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$
- Used in: home wiring, power distribution
- Advantage: Independent operation
- **Batteries in parallel:** Voltage stays same, capacity (mAh) adds for longer runtime

## Internal Resistance

Real-world power sources aren't perfect. Batteries and power supplies have internal resistance ( $r_{internal}$ ) that:

- Causes voltage to drop when supplying current:  $V_{actual} = V_{rated} - I \cdot r_{internal}$
- Limits maximum deliverable current
- Increases as batteries discharge or age
- Critical consideration for high-current robotics applications (motors, servos)
- Why you might see voltage "sag" when motors start

## Recommended Resources

- **All About Circuits** - Comprehensive free textbook: [www.allaboutcircuits.com](http://www.allaboutcircuits.com)
- **Khan Academy** - Electrical Engineering fundamentals with video tutorials
- **Falstad Circuit Simulator** - Interactive browser-based circuit simulator [www.falstad.com/circuit/](http://www.falstad.com/circuit/)

## Next Class Preview: Components, Schematics, & Breadboards

- **Components:** Resistors, capacitors, diodes, LEDs, switches, transistors
- **Schematics:** Reading circuit diagrams and symbols
- **Breadboard Layouts:** Translating schematics to physical builds
- **Hands-on:** Circuit assembly and troubleshooting
- **Datasheets:** Reading component specifications

*Practice makes perfect! Build circuits and experiment with different values.*